# WildEDS


Wildfire Early Detection System

Baldeep Pannu Joss Chandler


# **Table of Contents**

Table of Contents	2
System Design	3
System Schematic	4
PCB Design	5
РСВ Тор	5
PCB Bottom	6
PCB 3D Viewer	7
Bill of Materials	8
Part Selection Report	9
Assembly and Test Procedures	10
Final Status	11

# System Design

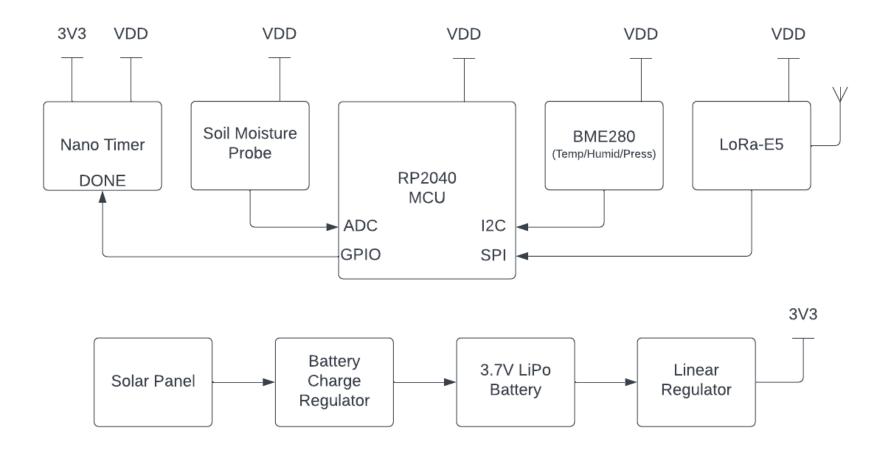



### **System Schematic**

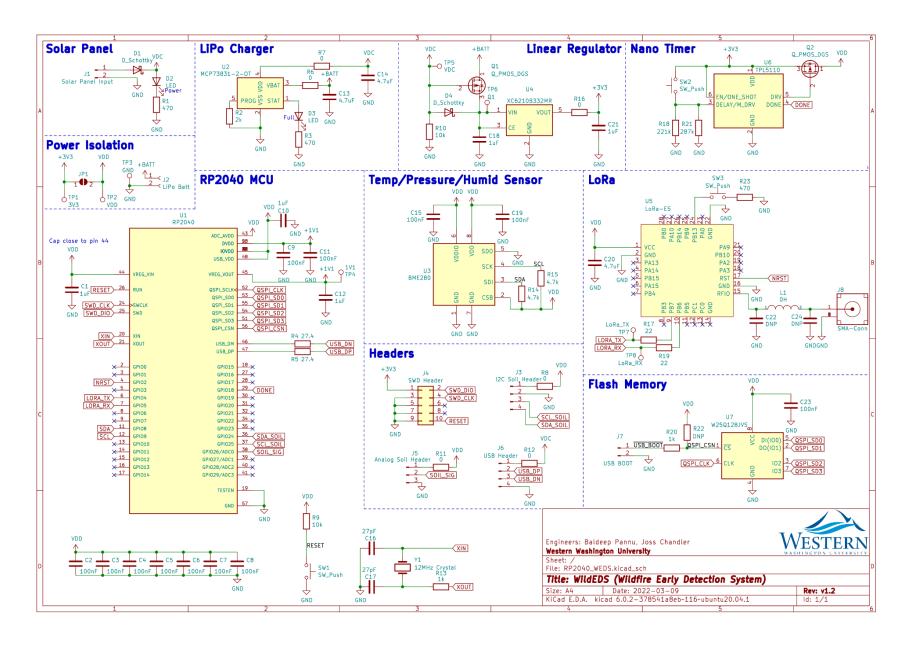


# PCB Design

# PCB Top

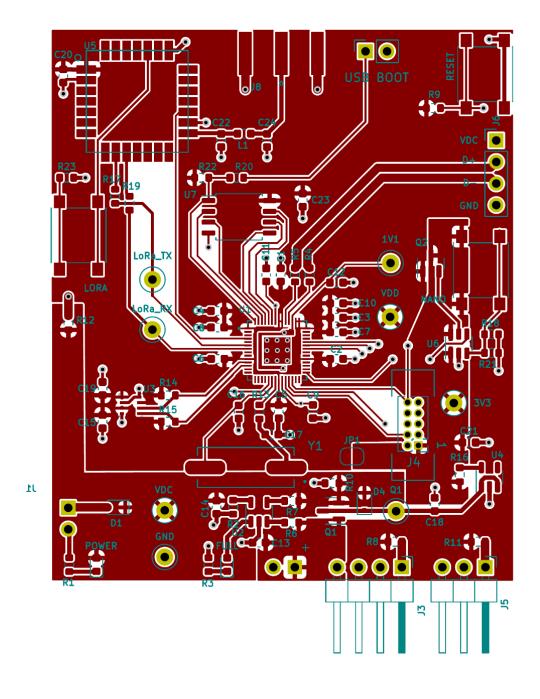

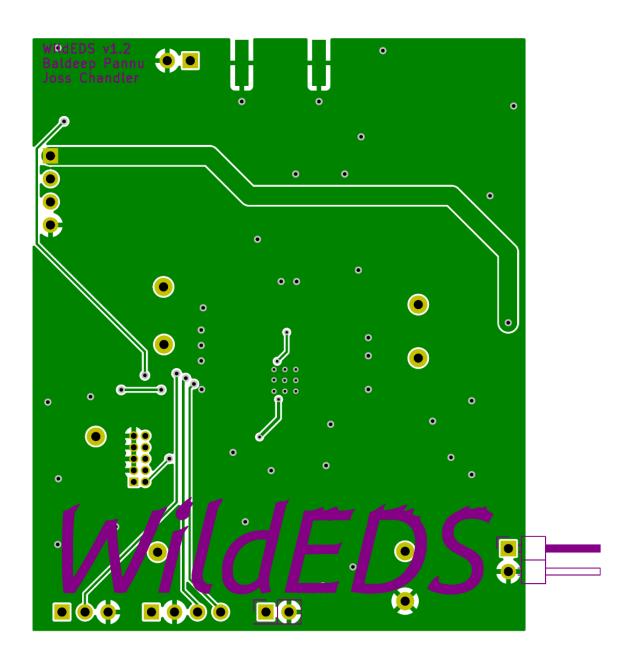

# PCB 3D Viewer

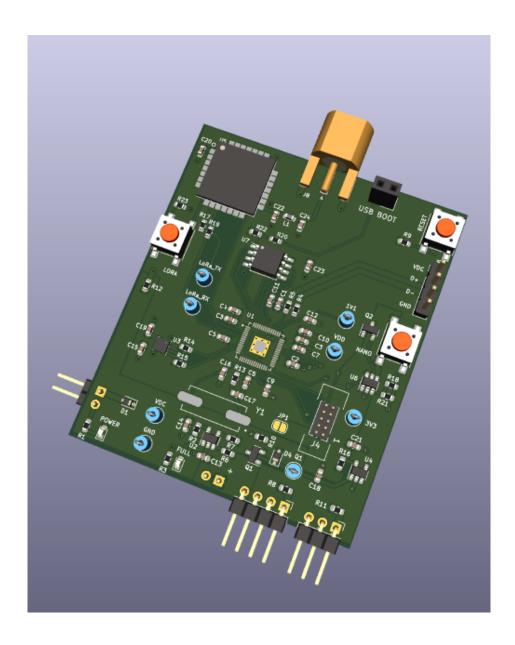

# **Bill of Materials**

References	Value	Footprint	MANUFACTURER	Quantity	
C2, C3, C4, C5, C6, C7, C8, C9, C11, C15, C19, C23	100nF	C_0603_1608Metric		<b>(</b> )	12
C1, C10, C12, C18, C21	1uF	C 0603 1608Metric			5
C13, C14, C20	4.7uF	C 0603 1608Metric			3
C16, C17	27pF	C_0603_1608Metric			2
C22, C24	DNP	C 0603 1608Metric			2
R6, R7, R8, R11, R12, R16	DIVIE	0 R 0603 1608Metric			6
R1, R3, R23	4.				3
		70 R_0603_1608Metric			2
R4, R5	10k	.4 R_0603_1608Metric			
R9, R10		R_0603_1608Metric			2
R13, R20	1k	R_0603_1608Metric			
R14, R15	4.7k	R_0603_1608Metric			2
R17, R19		22 R_0603_1608Metric			2
R2	2k	R_0603_1608Metric			1
R18	221k	R_0603_1608Metric			1
R21	287k	R_0603_1608Metric			1
R22	DNP	R_0603_1608Metric			1
L1	0H	L_0603_1608Metric			1
D1, D4	D_Schottky	D_SOD-323			2
D2, D3	LED	LED_0603_1608Metric			2
U1	RP2040	QFN40P700X700X90-57N	Raspberry Pi		1
U2	MCP73831-2-OT	SOT-23-5	Microchip		1
U3	BME280	Bosch_LGA-8_2.5x2.5mm_P0.65mm_ClockwisePinNumbering	Bosch		1
U4	XC6210B332MR	SOT-23-5	Torex		1
U5	LoRa-E5	LoRa-E5	Seeed		1
U6	TPL5110	SOT-23-6	Texas Instruments		1
U7	W25Q128JVS	SOIC-8 5.23x5.23mm P1.27mm	Winbond		1
Y1	12MHz Crystal	XTAL1140X470X420N	Abracon		1
SW1, SW2, SW3	SW_Push	SW_Push_1P1T_NO_6x6mm_H9.5mm			3
Q1, Q2	Q PMOS DGS	SOT-23			2
JP1	Power Isolation	SolderJumper-2_P1.3mm_Open_RoundedPad1.0x1.5mm			1
TP1	3V3	TestPoint Loop_D1.80mm_Drill1.0mm_Beaded			1
TP2	VDD	TestPoint Loop D1.80mm Drill1.0mm Beaded			1
TP3	GND	TestPoint Loop D1.80mm Drill1.0mm Beaded			1
TP4	1V1				1
		TestPoint_Loop_D1.80mm_Drill1.0mm_Beaded			1
TP5	VDC	TestPoint_Loop_D1.80mm_Drill1.0mm_Beaded			
TP6	Q1	TestPoint_Loop_D1.80mm_Drill1.0mm_Beaded			1
TP7	LoRa_TX	TestPoint_Loop_D1.80mm_Drill1.0mm_Beaded			1
TP8	LoRa_RX	TestPoint_Loop_D1.80mm_Drill1.0mm_Beaded			1
J1	Solar Panel Input	PinHeader_1x02_P2.54mm_Horizontal			1
J2	LiPo Batt	PinHeader_2x01_P2.54mm_Vertical			1
J3	I2C Soil Header	PinHeader_1x04_P2.54mm_Horizontal			1
J4	SWD Header	PinHeader_2x05_P1.27mm_Vertical			1
J5	Analog Soil Header	PinHeader_1x03_P2.54mm_Horizontal			1
J6	USB Header	PinHeader_1x04_P2.54mm_Vertical			1
J7	USB BOOT	PinSocket_1x02_P2.54mm_Vertical			1
J8	SMA-Conn	SMA_Amphenol_132289_EdgeMount_new	Samtec		1

### Assembly and Test Procedures

### Requirements:

The following are the required materials to assemble WildEDS:

- The design schematic
- Parts outlined on BOM
- Soldering station with:
  - Soldering Iron, Lead-Free Solder, Flux, Hot Air Soldering
    Station, Lead-Free Solder paste, Soldering oven, and Hot Plate

### Procedure:

- 1. Solar Panel & LiPo Charger:
  - a. Gather components: D1, D2, D3, R1, R2, R3, R6, R7, C13, C14, and U2
  - b. Solder U2 then D1, D2, D3, R1, R2, R3, R6, R7, C13, and C14 using the preferred soldering method.
  - c. Solder the solar panel in the J1 header using a soldering iron.
  - d. Connect the LiPo battery using the J2 header.
- 2. Linear Regulator:
  - a. Gather components: D4, Q1, R10, R16, C18, C21, and U4
  - b. Solder U4 then D4, Q1, R10, R16, C18, and C21 using the preferred soldering method.
  - c. Solder TP1, TP3, TP5, and TP6 using a soldering iron. Then solder the bridge at JP1.
  - d. Use TP 1 to verify output of 3V3.
  - e. Use TP 3 to verify the functionality of the ground.
  - f. Use TP 5 to verify the functionality of the Solar Panel.
  - g. Use TP 6 to verify the input to the linear regulator is between 3V5 and 4V2.
- 3. Nano Timer:
  - a. Gather components: Q2, SW2, R18, R21, and U6.
  - b. Solder U6 then Q2, R18, R21, and SW2 using the preferred soldering method.
  - c. Solder TP2 using a soldering iron.
  - d. Use SW2 and TP2 to verify the functionality of the nano timer.
- 4. RP2040 MCU:
  - a. Gather components: SW1, R4, R5, R9, R13, C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12, C16, C17, Crystal oscillator, and U1.
  - b. Solder U1 using the hot plate set to 200 degrees celsius and the hot air station.
  - c. Solder SW1, R4, R5, R9, R13, C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12, C16, C17, and the Crystal oscillator using preferred soldering method.
  - d. Solder TP1. will be used later to measure 1V1 from the MCU.
- 5. Flash Memory
  - a. Gather components: R20, C23, and U7
  - b. Solder U7 then R20 and C23 using the preferred soldering method. Do not populate R22.

c. Solder J7, the USB connector using a soldering iron.

#### 6. Lora Module:

- a. Gather components: SW3, R17, R19, R23, C20, the Antenna, and U5.
- b. Solder U5 using the hot plate set to 200 degrees celsius and the hot air station.
- c. Solder SW3, R17, R19, R23, and C20 using the preferred soldering method. Do not populate L1, C22, and C24.
- d. Attach the antenna to J8.
- e. TP7 and TP8 shall be used later to verify the proper functionality of the LoRa Module.

### 7. Temp/Pressure/Humid Sensor:

- a. Gather components: R14, R15, C15, C19, and U3.
- b. Solder U3 then solder R14, R15, C15, and C19 using the preferred soldering method.

#### 8. Headers:

- a. Gather components: R8, R11, R12, J3, J4, J5, and J7.
- b. Solder R8, R11, 12 using the preferred soldering method.
- c. Solder J3, J4, J5, and J7 using a soldering iron.
- d. Connect a USB cable into J6 and verify the functionality of the MCU and LoRa module using software and TP1, TP7, and TP8.

### Considerations:

Use caution when soldering the MCU and LoRa module as it may overheat.

Avoid using hot air near Headers to avoid melting header.

Practice good solder technique and safety.